 


Verilog Assignment 3
27.08.2024


Verilog Assignment: Structural Modeling for Routing and Error Correction

- a) Write a Verilog module for single-bit error correcting router module **secure_router**, as shown in the diagram below:




The module takes a 6-bit input **d_in**, where the first 2-bits indicate the output port number, and the last 4-bits indicate data. Using Hamming code for single-bit error correction, the 4-bit data input is converted to a 7-bit Hamming-coded data output, and is sent over one of the output ports depending on the first 2-bits of **d_in**.

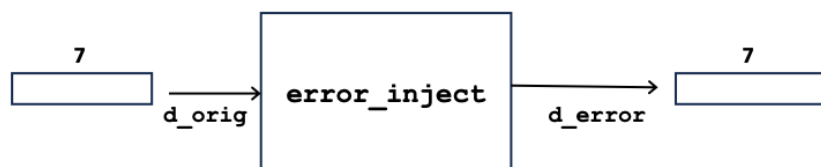
- b) Write a Verilog module **error_inject**, as shown in the diagram below, which takes a 7-bit data as input, injects a single bit error in the data, and sends it to the 7-bit output port.



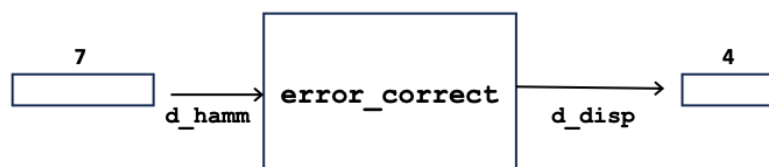- c) Write a Verilog module **error_correct**, as shown in the diagram below, which takes a 7-bit Hamming-coded data as input, corrects single-bit errors (if any), and sends the corrected 4-bit data to the output port.



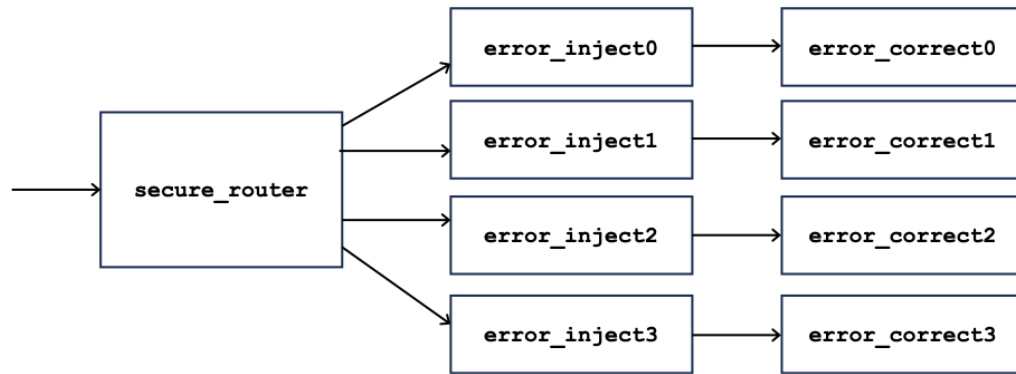- d) Write a top-level Verilog module as shown below, which instantiates the various Verilog modules as indicated.



- e) Write a test bench to simulate the operation of the design and verify its correctness. Apply various 6-bit inputs to the **secure_router** module, so that the data gets routed to various output ports.
- f) Generate the bit-map file, download it on the FPGA board, and demonstrate the working of the circuit. The outputs from the **error_correct** modules must be displayed in suitable fashion.

Assume that all circuit operations are carried out in synchronism with a clock (not shown). Make relevant assumptions where necessary.

Extend the routing and error correction assignment as follows:

a) When the "secure_router", "error_inject" and "error_correct" modules communicate, they shall do so by transmitting/receiving the bits serially. Each communication channel will have two signals, a 1-bit data signal, and a 1-bit strobe signal. A complete pulse will be sent over the strobe signal whenever the next data bit is ready. The receiver will read the bits serially triggered by the "edge" of the strobe signal.

b) Suppose that the first 2-bits in "d_in" indicate the destination router number (assume there are four routers). Each router will have a routing table containing entries as follows: <destination number, output port number>. Draw the schematic diagram of a scenario with four routers with connections between them. The input data packet must be correctly forwarded to the destination router.
